

AHSANULLAH UNIVERSITY OF SCIENCE AND TECHNOLOGY

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

LAB REPORT

COURSE NO : EEE 2226

COURSE NAME : Numerical Technique Laboratory

EXPERIMENT NO : 01

DATE OF SUBMISSION : 14/07/2025

Submitted by:

Name : Rafayet Ahammad


ID : 20230105206

 $Year \qquad : 2^{nd}$

 $Semester \ : 2^{nd}$

Section : D(2)

Exercise 1. Find the value of $y = \ln(\sinh(e^{\frac{6\pi}{543}}))$

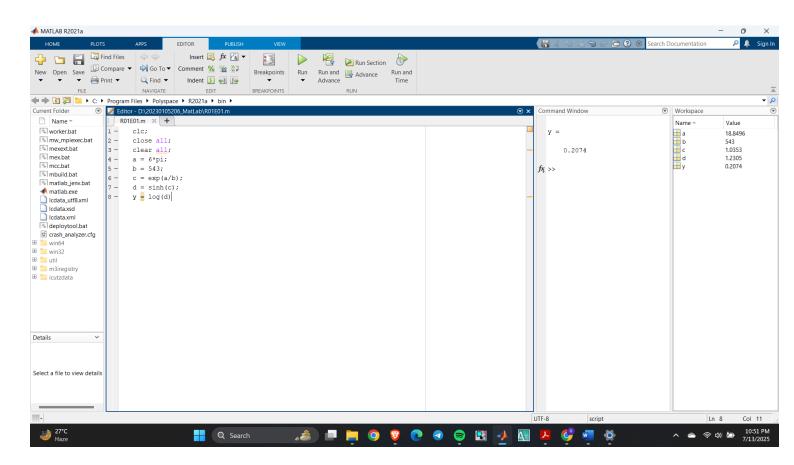


Exercise 2:

(a) Find the size, and length of following matrices A=[1 2 3; 4 5 6; 7 6 54; 65 23 45] B=7:1:13.5

(b) Determine submatrix C and D from A. C=[23;654;2345]


D=[4 5 6]

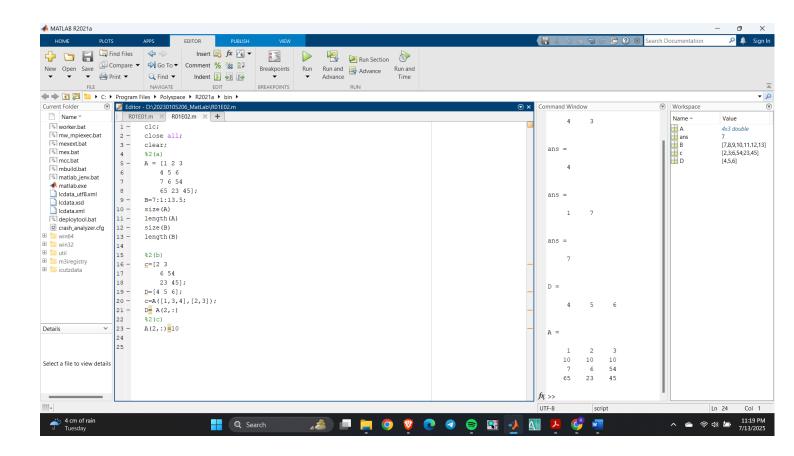(c) Replace all the value of 2nd row into 10 and display the matrix A.



#Exercise 3.

A=[2 3; 4 5]; B=[3 4; 6 7]; Find A+B, A*B, A.*B, A/B, A\B, A.^2, A./B

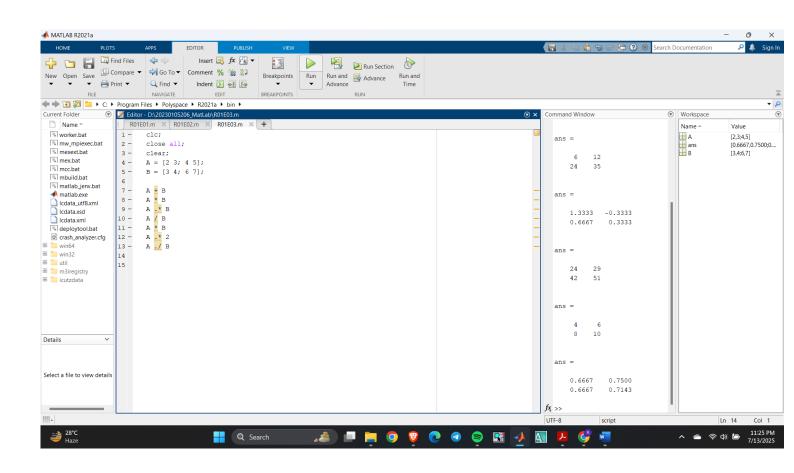

Exercise 4.

Define the matrices
A=[17 2 3 4; 5 6 7 8; 9 10 11 12; 13 14 15 16]
B=[2 3 4 5; 6 7 8 9; 10 11 12 13; 14 15 16 17]
C=[1 2 3; 4 5 6; 7 8 9]
y=[4 3 2 1]'

Note the transpose ' on the y-vector which makes y a column vector.

- a) Compute AB and BA. Is matrix multiplication commutative?
- b) Compute AC. Why do you get an error message?

♠ MATLAB R2021a Find Files Insert 🛃 fx 👍 ▼ 🕂 🗀 🔚 · 14 Compare ▼ Go To ▼ Comment % % % *? Breakpoints ~ Run Run and Advance Advance 🚔 Print ▼ Q Find ▼ Indent 🛐 🚭 🔯 🔷 🖈 🔃 🞾 🗀 🕨 C: 🕨 Program Files 🕨 Polyspace 🕨 R2021a 🕨 bin 🕨 Current Folder
Name Command Window R01E01.m × R01E02.m × R01E03.m × R01E04.m × + A AB 4x4 double mw_mpiexec.bat close all; 4x4 double 4x4 double 4x4 double 4x4 double [1,2,3;4,5,6;7,8,9] clear; A=[17 2 3 4; 5 6 7 8; 9 10 11 12; 13 14 15 16]; mexext.bat mex.bat mex.bat mex.bat mex.bat mbuild.bat 228 254 280 306 B=[2 3 4 5; 6 7 8 9; 10 11 12 13; 14 15 16 17]; C=[1 2 3; 4 5 6; 7 8 9]; 440 542 matlab_jenv.bat
matlab_jenv.bat
matlab.exe
lcdata_utf8.xml
lcdata.xsd
lcdata.xml 484 600 658 [4:3:2:1] y=[4 3 2 1]'; BA = deploytool.bat crash_analyzer.cfg 11 isequal(AB, BA); 132 146 160 % as AB # BA Matrix multiplication is NOT commutative 260 win64 win32 502 388 434 480 % The operation A * C will fail due to dimension mismatch (as noted in the original output) 15 ⊞ icutzdata variable 'c' Error in **R01E04** (line 14) fx >> Select a file to view details 👯 Q Search 🔏 🔲 📜 🧿 🦁 🕢 🔞 🖼 📣 4

3

Exercise 5.

(a) Solve the following system of equations:


$$17x_1+2x_2+3x_3+4x_4=4$$

$$5x_1+6x_2+7x_3+8x_4=3$$

$$9x_1+10x_2+11x_3+12x_4=2$$

$$13x_1+14x_2+15x_3+16x_4=1$$

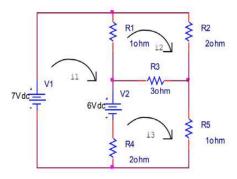(b) Solve the following circuit to find i1, i2, and i3.



Ans: i1= 3 amp, i2= 2 amp, i3= 3 amp.

For (b) using mesh analysis,

Loop_1: 3i1 - i2 - 2i3 = 1 Loop_2: i1 - 6i2 + 3i3 = 0 Loop_3: 2i1 + 3i2 - 6i3 = -6

